

Circuit Analysis

Read from **Lesson 4** of the **Current Electricity** chapter at **The Physics Classroom**:


<http://www.physicsclassroom.com/Class/circuits/u9l4b.html>

<http://www.physicsclassroom.com/Class/circuits/u9l4c.html>

<http://www.physicsclassroom.com/Class/circuits/u9l4d.html>

MOP Connection: Electric Circuits: sublevel 11

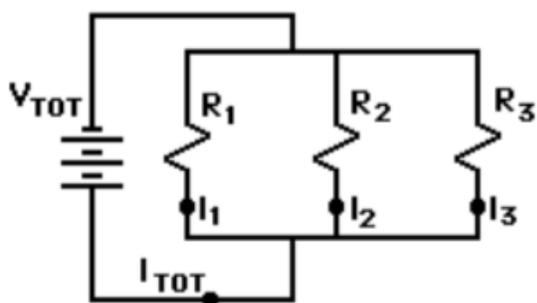1. Fill in the blanks in the following diagram. Show appropriate units.



$R_{Tot} =$ _____ $I_{Tot} =$ _____

$\Delta V_1 =$ _____ $I_1 =$ _____


$\Delta V_2 =$ _____ $I_2 =$ _____

$\Delta V_3 =$ _____ $I_3 =$ _____

$V_{Tot} = 60.0 \text{ V}$

$R_1 = 12.5 \ \Omega$ $R_2 = 14.7 \ \Omega$ $R_3 = 19.1 \ \Omega$

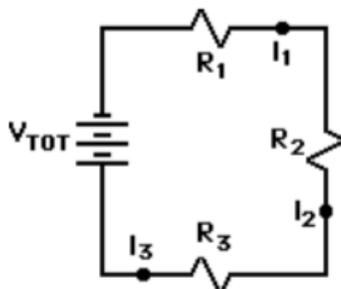2. Fill in the blanks in the following diagram. Show appropriate units.



$R_{Tot} =$ _____ $I_{Tot} =$ _____

$\Delta V_1 =$ _____ $I_1 =$ _____


$\Delta V_2 =$ _____ $I_2 =$ _____

$\Delta V_3 =$ _____ $I_3 =$ _____

$V_{Tot} = 60.0 \text{ V}$

$R_1 = 12.5 \ \Omega$ $R_2 = 14.7 \ \Omega$ $R_3 = 19.1 \ \Omega$

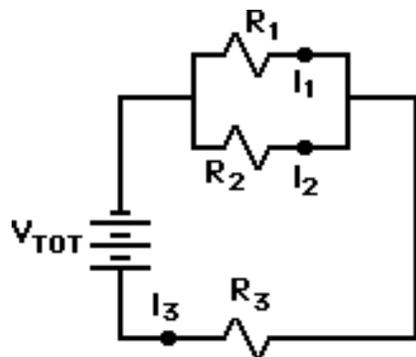3. Fill in the blanks in the following diagram. Show appropriate units.



$R_{Tot} =$ _____ $I_{Tot} =$ _____

$\Delta V_1 =$ _____ $I_1 =$ _____

$\Delta V_2 =$ _____ $I_2 =$ _____

$\Delta V_3 =$ _____ $I_3 =$ _____

$V_{Tot} = 120.0 \text{ V}$

$R_1 = 16.0 \ \Omega$ $R_2 = 16.0 \ \Omega$ $R_3 = 6.0 \ \Omega$