

## Electric Circuits Auxilliary Items


### For Voltage-Current-Resistance Lab

(Tape the following into your Data section and complete.)

Data:


Resistor #1:  $R = \underline{\hspace{2cm}}$   $\Omega$  (based on color code)

# of Batteries	$\Delta V$ (Volts)	I (Amps)
1		
2		
3		
4		

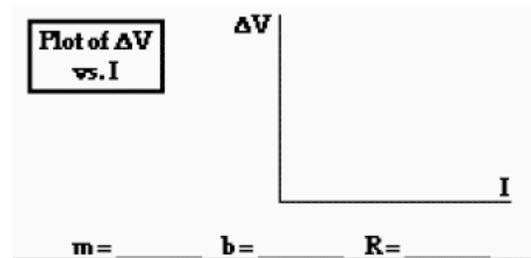

Resistor #2:  $R = \underline{\hspace{2cm}}$   $\Omega$  (based on color code)

# of Batteries	$\Delta V$ (Volts)	I (Amps)
1		
2		
3		
4		

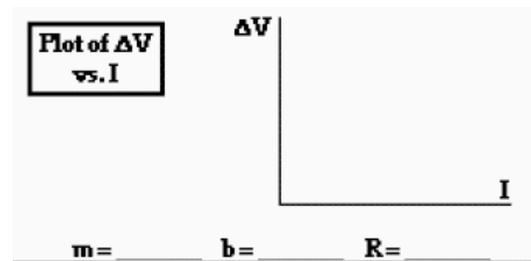







### For Combination Circuits Lab

(Tape the following into your Data section and complete.)

Data:

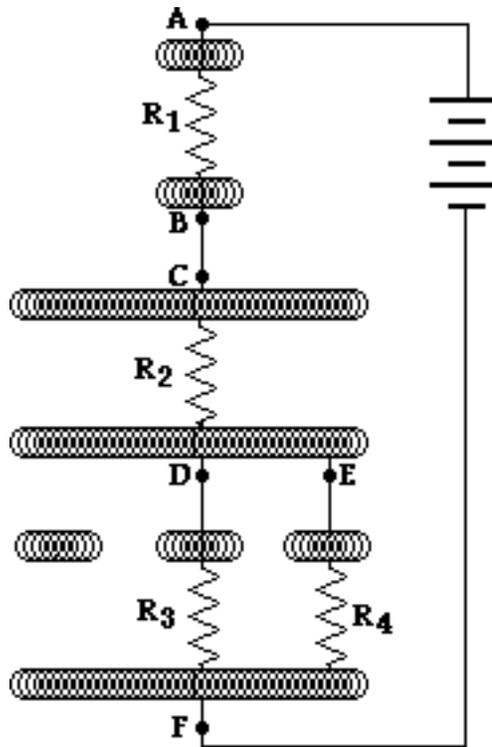

Record voltmeter readings

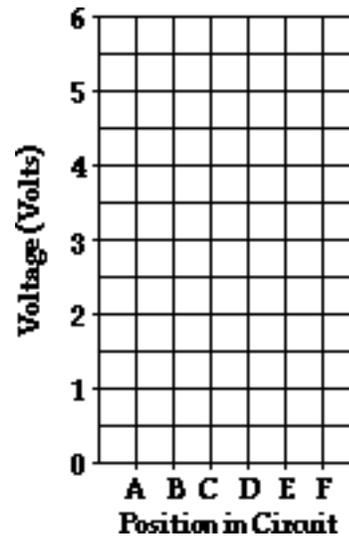

	Measured Current (A)	Measure $\Delta V$ (V)	Calculated Resistance ( $\Omega$ )	Theoretical Resistance ( $\Omega$ ) -color bands-	Percent Error
R <sub>1</sub>			$\Delta V/I =$		
R <sub>2</sub>			$\Delta V/I =$		
R <sub>3</sub>			$\Delta V/I =$		
R <sub>4</sub>			$\Delta V/I =$		
Total (Battery )			$\Delta V_{tot}/I_{tot} =$	$R_{eq} =$ (use eq'n)	

Clearly show your calculations for the resistance (in cells) and the percent error (using calculated and theoretical resistance values) for each of the four resistors.